

I. Procedure

A. Task #1

First, I drew out the 2-output / 3-input state diagram for the entrance passcode as shown in Figure 1. Then, I first do the FSM code for “passcode.sv” at first. It’s a 9-state Moore FSM.

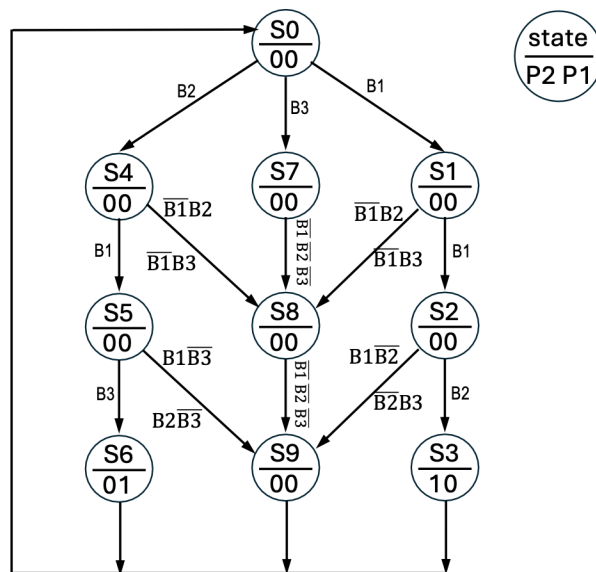


Figure 1: Moore finite state machine of “passcode” module.

Second, I worked on the counter which is “counter.sv” for counting how many cars have been entranced the parking lot.

Third, I used “twoDFF.sv” and which is a D flip-flop code from my EE271 previous lab and also “unserInput.sv” for holding the value that it will only count one time when KEY[3:1] is pressed, no matter how long it pressed (during many clock cycles).

The HDL code “userInput.sv is also contributed by a FSM, and Figure 2 shows the state diagram of the Moore finite-state machine for this module.

 


Figure 2: Moore finite state machine of “userInput” module.

Third, I created a higher-level file to integrate “passcode.sv”, “twoDFF.sv”, and “userInput.sv” which is passcode_all.sv.

Fourth, I contributed passcode_all_counter.sv, to implement calling “counter” method for counting number of cars entering the parking lots and sync with “passcode_all.sv”.

The trigger condition “dec” needs to go through the “twoDFF” module and the “userInput” module, so that it will not over count when the signal is stay HIGH in many clock cycles.

Fifth, I wrote “bcd7seg.sv” to driving the seven-segment displays HEX5, HEX4, HEX3, HEX2, HEX1, and HEX0.

Sixth, I contributed “top_cell.sv” for integrating “passcode_all_counter.sv” and “bcd7seg.sv”.

Seventh, I finished “DE1_SoC.sv” main code, which is easily call the method “top_cell”; however, when I tested it on LabsLand, the entrance gate was not working with it. So, I tried to add “signal_extender.sv” given by Canvas. Then, pull out the entrance gate signal which is for V_GPIO[31] to extend.

GPIO Ports	I/O	Description
V_GPIO[28]	I	Presence Parking 1: Lets you know if there is a car in parking spot 1.
V_GPIO[29]	I	Presence Parking 2: Lets you know if there is a car in parking spot 2.
V_GPIO[30]	I	Presence Parking 3: Lets you know if there is a car in parking spot 3.
V_GPIO[23]	I	Presence at Entrance Gate: Lets you know if there is a car waiting at the entrance
V_GPIO[24]	I	Presence at Exit Gate: Lets you know if there is a car waiting at the exit.
V_GPIO[26]	O	LED Parking 1: Lets you change LED color of parking spot 1 (0 = green, 1 = red).
V_GPIO[27]	O	LED Parking 2: Lets you change LED color of parking spot 2 (0 = green, 1 = red).
V_GPIO[32]	O	LED Parking 3: Lets you change LED color of parking spot 3 (0 = green, 1 = red).
V_GPIO[34]	O	LED Full: Lets you change LED color of the full indicator LED (0 = green, 1 = red).
V_GPIO[31]	O	Open Entrance Gate: Opens the entrance gate. When you send a 1, the gate will stay open until a car enters the lot.
V_GPIO[33]	O	Open Exit Gate: Opens the exit gate. When you send a 1, the gate will stay open until a car leaves the lot.

Table 1: GPIO mapping and port descriptions.

II. Result

A. Task #1

So, what I did for testbench is test if I pressed “KEY2, KEY1, KEY3”, “KEY1, KEY1, KEY2” in order when there is a car waiting at entrance gate, and I see what happened with all the modules. After those, I checked when the car is leaving for a few times for checking if the counter and others module work as I thought. Figure 3 shows the simulated waveform of the 3D parking lot simulator

generated by Modelsim. For the demonstration of this design, I provide the recorded video. Please access the video via the hyperlink: https://www.youtube.com/watch?v=0ZIBwFXs_O8 .

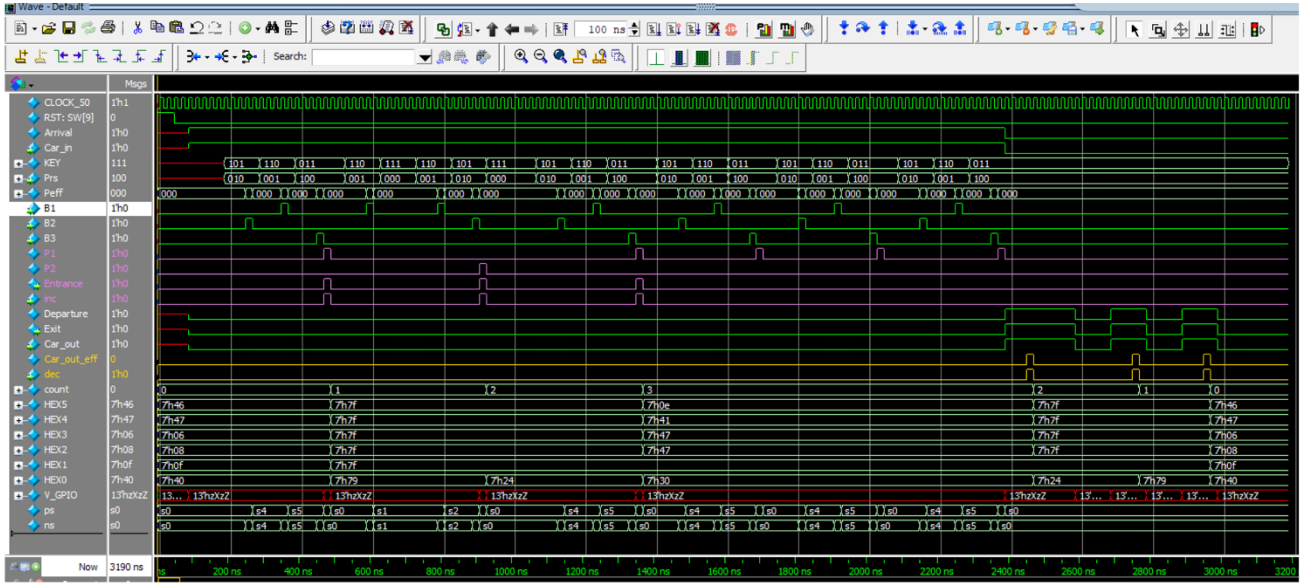


Figure 3: The simulated waveform of the 3D parking lot simulator generated by Modelsim.

III. Final Product

In this LAB, I became familiar with the GPIO interface and the LabsLand environment. The experimental results showed that by combining FPGA and GPIO, I could successfully control the parking and vehicle entry and exit status in the 3D parking lot simulator.

IV. Appendix

A. Block diagram

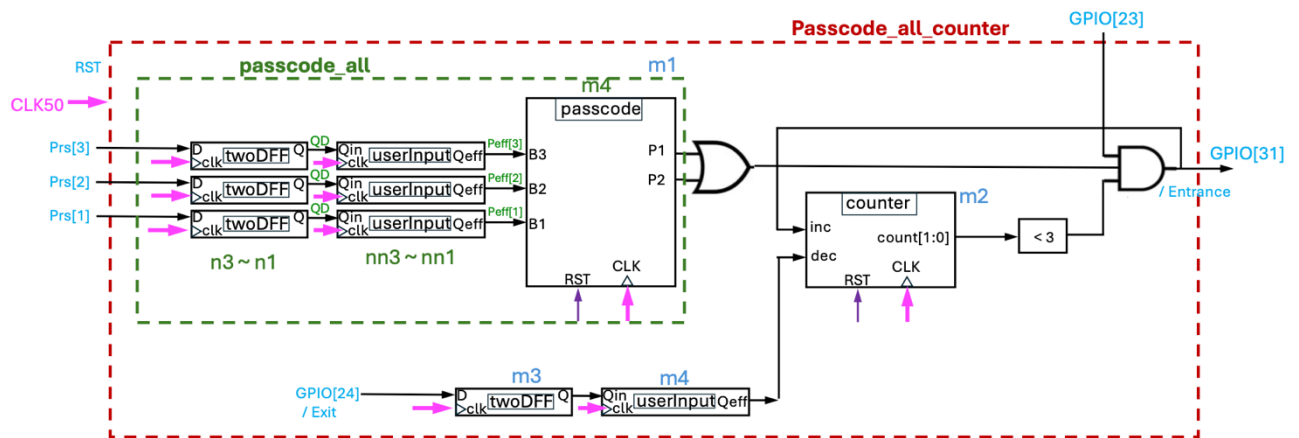


Figure 4: The block diagram of the module “passcode_all_counter”.

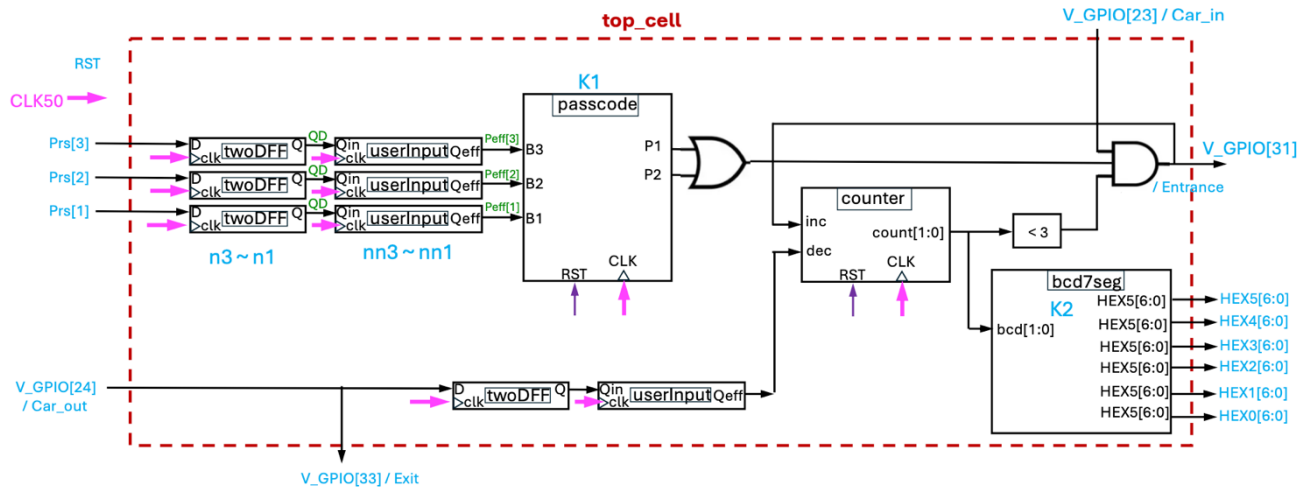


Figure 5: The block diagram of the module “top_cell”.

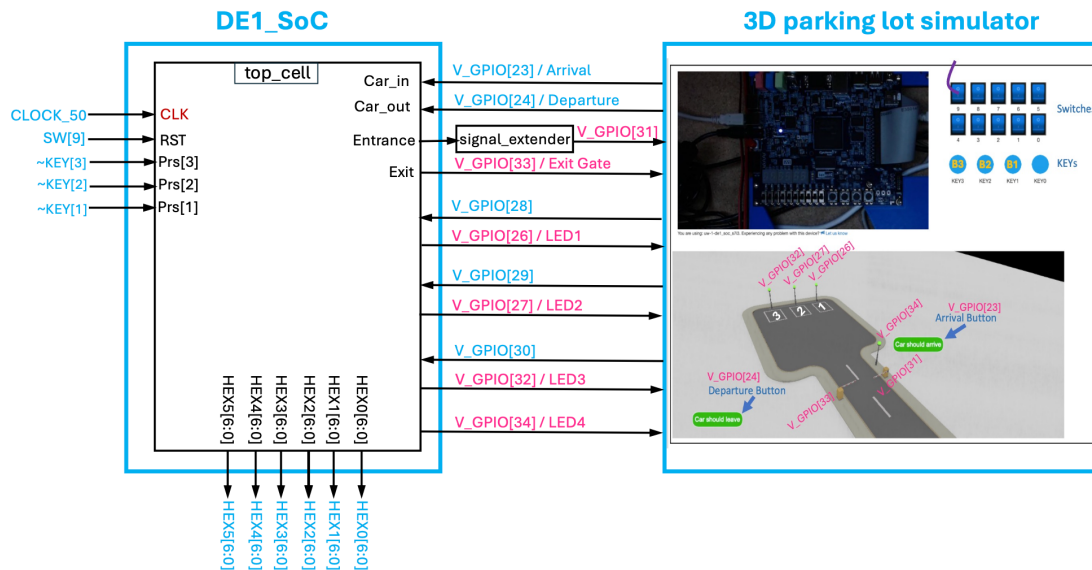


Figure 6: The block diagram of the whole design.

B. DE1_SoC.sv

```
6  module DE1_SoC(HEX5, HEX4, HEX3, HEX2, HEX1, HEX0, KEY, SW, LEDR, V_GPIO, CLOCK_50);
7  // define ports
8      output logic [6:0]  HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
9      output logic [9:0]  LEDR;
10     input logic [3:1]   KEY;
11     input logic [9:0]   SW;
12     input logic CLOCK_50;
13     inout logic [35:23] V_GPIO;
14
15     logic hold, hold2; // for signal_extender
16
17     top_cell top (.CLK(CLOCK_50), .RST(SW[9]), .Prs(~KEY),
18                 .Car_in(V_GPIO[23]), .Car_out(V_GPIO[24]),
19                 .Entrance(hold), .Exit(V_GPIO[33]),
20                 .HEX5, .HEX4, .HEX3, .HEX2, .HEX1, .HEX0);
21
22     signal_extender s1(.in(hold), .out(hold2), .reset(SW[9]), .clk(CLOCK_50));
23
24     assign V_GPIO[31] = hold2;
25     assign V_GPIO[26] = V_GPIO[28]; // specify the color of LED1.
26     assign V_GPIO[27] = V_GPIO[29]; // specify the color of LED2.
27     assign V_GPIO[32] = V_GPIO[30]; // specify the color of LED3.
28
29     // specify the color (0:green / 1:red) of the full indicator LED.
30     assign V_GPIO[34] = V_GPIO[28] & V_GPIO[29] & V_GPIO[30];
31
32     endmodule // DE1_SoC
33
```

C. top_cell.sv

```
1  module top_cell (CLK, RST, Prs, Car_in, Car_out, Entrance, Exit, HEX5, HEX4, HEX3, HEX2,
2  HEX1, HEX0);
3      input logic CLK, RST;
4      input logic [3:1] Prs;
5      input logic Car_in, Car_out;
6      output logic Entrance, Exit;
7      output logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
8      logic [1:0] count;
9
10     passcode_all_counter K1 (.CLK, .RST, .Prs, .Car_in, .Car_out, .Entrance, .Exit,
11     .count);
12     bcd7seg                K2 (.bcd(count), .HEX5, .HEX4, .HEX3, .HEX2, .HEX1, .HEX0);
13
14     endmodule
```

D. passcode_all_counter.sv

```
1  module passcode_all_counter (CLK, RST, Prs, Car_in, Car_out, Entrance, Exit, count);
2      input logic CLK, RST;
3      input logic [3:1] Prs;
4      input logic Car_in, Car_out;
5      output logic Entrance, Exit;
6      output logic [1:0] count;
7
8      logic Car_out_QD, Car_out_eff;
9      logic P1, P2;
10
11     assign Entrance = Car_in & (P1 | P2) & (count < 3);
12
13     assign Exit = Car_out;
14
15     passcode_all m1 (.CLK(CLK), .RST(RST), .Prs(Prs), .P2(P2), .P1(P1));
16     counter      m2 (.clk(CLK), .reset(RST), .inc(Entrance), .dec(Car_out_eff),
17     .count(count));
18     twoDFF       m3 (.CLK(CLK), .RST(RST), .D(Car_out), .Q(Car_out_QD));
19     userInput    m4 (.CLK(CLK), .RST(RST), .Qin(Car_out_QD), .Qeff(Car_out_eff));
20 endmodule
21
```

E. bcd7seg.sv

```
6 module bcd7seg(bcd, HEX5, HEX4, HEX3, HEX2, HEX1, HEX0);
7 input logic [1:0] bcd;
8 output logic [6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
9
10 parameter [6:0] Blank = 7'b111_1111; // 7'h7f
11 parameter [6:0] A = 7'b000_1000; // 7'h08
12 parameter [6:0] C = 7'b100_0110; // 7'h46
13 parameter [6:0] E = 7'b000_0110; // 7'h06
14 parameter [6:0] F = 7'b000_1110; // 7'h0e
15 parameter [6:0] L = 7'b100_0111; // 7'h47
16 parameter [6:0] r = 7'b000_1111; // 7'h0f
17 parameter [6:0] U = 7'b100_0001; // 7'h41
18 parameter [6:0] Chr_0 = 7'b100_0000; // 7'h40
19 parameter [6:0] Chr_1 = 7'b111_1001; // 7'h79
20 parameter [6:0] Chr_2 = 7'b010_0100; // 7'h24
21 parameter [6:0] Chr_3 = 7'b011_0000; // 7'h30
22
23 always_comb begin
24 case(bcd)
25 3'b000: {HEX5, HEX4, HEX3, HEX2, HEX1, HEX0} = {C, L, E, A, r, Chr_0};
26 3'b001: {HEX5, HEX4, HEX3, HEX2, HEX1, HEX0} = {Blank, Blank, Blank, Blank, Blank,
Chr_1};
27 3'b010: {HEX5, HEX4, HEX3, HEX2, HEX1, HEX0} = {Blank, Blank, Blank, Blank, Blank,
Chr_2};
28 3'b011: {HEX5, HEX4, HEX3, HEX2, HEX1, HEX0} = {F, U, L, L, Blank, Chr_3};
29 default: {HEX5, HEX4, HEX3, HEX2, HEX1, HEX0} = {Blank, Blank, Blank, Blank, Blank,
Blank};
30 endcase
31 end
32
33 endmodule
```

F. passcode_all.sv

```
1 module passcode_all (CLK, RST, Prs, P2, P1);
2 input logic CLK, RST;
3 input logic [3:1] Prs;
4 output logic P2, P1;
5
6 logic [3:1] QD, Peff;
7
8 twoDFF n3 (.CLK(CLK), .RST(RST), .D(Prs[3]), .Q(QD[3]));
9 twoDFF n2 (.CLK(CLK), .RST(RST), .D(Prs[2]), .Q(QD[2]));
10 twoDFF n1 (.CLK(CLK), .RST(RST), .D(Prs[1]), .Q(QD[1]));
11 userInput nn3 (.CLK(CLK), .RST(RST), .Qin(QD[3]), .Qeff(Peff[3]));
12 userInput nn2 (.CLK(CLK), .RST(RST), .Qin(QD[2]), .Qeff(Peff[2]));
13 userInput nn1 (.CLK(CLK), .RST(RST), .Qin(QD[1]), .Qeff(Peff[1]));
14
15 passcode m4 (.CLK(CLK), .RST(RST), .B3(Peff[3]), .B2(Peff[2]), .B1(Peff[1]), .P2(P2),
.P1(P1));
16
17 endmodule
```

G. counter.sv

```
1  module counter(clk, reset, inc, dec, count);
2
3      input logic clk, reset, inc ,dec;
4      output logic [1:0] count;
5
6      //counter logic
7
8      always_ff @(posedge clk or posedge reset) begin
9          if (reset)
10             count <= 2'b00; // reset count to 0
11
12         else begin
13             if (inc && !dec && count < 2'b11)
14                 count <= count + 1; // Increment if below max
15
16             else if (dec && !inc && count > 2'b00)
17                 count <= count - 1; // Decrement iff above 0
18
19         end
20     end
21
22 endmodule
23
```

H. twoDFF.sv

```
6  module twoDFF (CLK, RST, D, Q);
7      input logic CLK, RST;
8      input logic D;
9      output logic Q;
10     logic Q1;
11
12     // DFFs
13     always_ff @(posedge CLK or posedge RST) begin
14         if (RST) begin
15             Q <= 0;
16             Q1 <=0;
17         end
18         else begin
19             Q <= Q1;
20             Q1 <= D;
21         end
22     end
23
24 endmodule
25
```

I. userInput.sv

```
5 / ----- /
6 module userInput (CLK, RST, Qin, Qeff);
7 input logic CLK, RST;
8 input logic Qin;
9 output logic Qeff;
10
11 // State variables
12 typedef enum logic [1:0] {
13     start, s1, s2
14 } state_t;
15 state_t ps, ns;
16
17 // Next State logic
18 always_comb begin
19     ns = start; // Default to avoid latches
20     case (ps)
21         start: if (Qin == 1) ns = s1;
22                else ns = start;
23
24         s1:    if (Qin == 1) ns = s2;
25                else ns = start;
26
27         s2:    if (Qin == 1) ns = s2;
28                else ns = start;
29         default: ns = start;
30     endcase
31 end
32
33 // Output logic
34 always_comb begin
35     Qeff = 0; // Default to avoid latches
36     case (ps)
37         start: Qeff = 0;
38         s1:    Qeff = 1;
39         s2:    Qeff = 0;
40         default: Qeff = 0;
41     endcase
42 end
43
44 // DFFs
45 always_ff @(posedge CLK or posedge RST) begin
46     if (RST)
47         ps <= start;
48     else
49         ps <= ns;
50 end
51
52 endmodule
53
```


J. passcode.sv

```
1  module passcode (CLK, RST, B3, B2, B1, P2, P1);
2      input logic CLK, RST, B3, B2, B1;
3      output logic P2, P1;
4
5      // State variables
6      typedef enum logic [3:0] {
7          s0, s1, s2, s3, s4, s5, s6, s7, s8, s9
8      } state_t;
9      state_t ps, ns;
10
11     // assign ps_out = ps;
12
13     // Next State logic
14     always_comb begin
15         ns = s0; // Default to avoid latches
16         case (ps)
17             s0: if (B1 == 1)
18                     ns = s1;
19                 else if (B2 == 1)
20                     ns = s4;
21                 else if (B3 == 1)
22                     ns = s7;
23                 else ns = s0;
24
25             s1: if (B1 == 1)
26                     ns = s2;
27                 else if ((B2 == 1) || (B3 == 1))
28                     ns = s8;
29                 else ns = s1;
30
31             s2: if (B2 == 1)
32                     ns = s3;
33                 else if ((B1 == 1) || (B3 == 1))
34                     ns = s9;
35                 else ns = s2;
36
37             s3: ns = s0;
38
39             s4: if (B1 == 1)
40                     ns = s5;
41                 else if ((B2 == 1) || (B3 == 1))
42                     ns = s8;
43                 else ns = s4;
44
45             s5: if (B3 == 1)
46                     ns = s6;
47                 else if ((B1 == 1) || (B2 == 1))
48                     ns = s6;
49                 else ns = s5;
50
51             s6: ns = s0;
52
53             s7: if ((B1 == 0) && (B2 == 0) && (B3 == 0))
54                     ns = s7;
55                 else
56                     ns = s8;
57
58             s8: if ((B1 == 0) && (B2 == 0) && (B3 == 0))
59                     ns = s8;
60                 else
61                     ns = s9;
62
63             s9: ns = s0;
64
65             default: ns = s0;
66         endcase
67     end
68
69     // Output logic
70     always_comb begin
71         {P2, P1} = 2'b00; // Default to avoid latches
72         case (ps)
73             s0: {P2, P1} = 2'b00;
74             s1: {P2, P1} = 2'b00;
75             s2: {P2, P1} = 2'b00;
```

```

76         s3: {P2, P1} = 2'b10;
77         s4: {P2, P1} = 2'b00;
78         s5: {P2, P1} = 2'b00;
79         s6: {P2, P1} = 2'b01;
80         s7: {P2, P1} = 2'b00;
81         s8: {P2, P1} = 2'b00;
82         s9: {P2, P1} = 2'b00;
83         default: {P2, P1} = 2'b00;
84     endcase
85 end
86 // DFFs
87
88 always_ff @(posedge CLK or posedge RST) begin
89     if (RST)
90         ps <= s0;
91     else
92         ps <= ns;
93 end
94
95 endmodule
96

```